

RLC Series Circuit

Example 3.1.1. Find the amplitude, u_m , rms value, U , angular frequency, ω , frequency, f , period, T and phase angle, ϕ of the sinusoidal voltage: $u(t) = 15 \cos(100t - 35^\circ) \text{ V}$.

Solution:

Analyzing the sinusoidal voltage function, we have: the amplitude $u_m=15\text{V}$; the rms value $U = \frac{u_m}{\sqrt{2}} = 10.60\text{V}$; the angular frequency is $\omega=100 \text{ rad/s}$; the frequency $f = \frac{\omega}{2\pi} = 15.92 \text{ Hz}$; the period $T = \frac{1}{f} = \frac{2\pi}{\omega} = 0.0628 \text{ s} = 62.8 \text{ ms}$; the phase angle $\phi = -35^\circ$.

Example 3.1.2. Calculate the phase angle between $u_1(t) = -10 \cos(\omega t + 40^\circ)$ and $u_2(t) = 12 \sin(\omega t - 20^\circ)$.

Solution:

In order to compare u_1 and u_2 , we have to express both functions in the same form, i.e. in terms of sin functions. Using the identity $-\cos \alpha = \sin(\alpha - 90^\circ)$, we can write $u_1(t) = 10 \sin(\omega t + 40^\circ - 90^\circ) = 10 \sin(\omega t - 50^\circ)$. Comparing now both functions, the phase angle between the two functions is $\phi_{12} = \phi_1 - \phi_2 = -50^\circ - (-20^\circ) = -30^\circ$. We say that the $u_1(t)$ lags the $u_2(t)$ by the angle of 30° , or conversely, the $u_2(t)$ leads the $u_1(t)$ by the angle of 30° .

Example 3.1.3. A sinusoidal current at the moment $t=0$ has the value $i(0)=5\text{A}$ and at $t_1=2.5 \text{ ms}$ reaches peak value. Knowing the period $T=20 \text{ ms}$, calculate: a) the phase angle, ϕ ; the instantaneous form of the sinusoidal current, $i(t)$.

Solution:

We will consider a sinusoidal current in form $i(t) = i_m \sin(\omega t + \phi)$. For $t_1=2.5 \text{ ms}$ the function reaches the peak, means that $\sin(\omega t_1 + \phi) = 1$, and as a consequence $\omega t_1 + \phi = \frac{\pi}{2}$, and $\phi = \frac{\pi}{2} - \omega t_1 = \frac{\pi}{2} - \frac{2\pi}{T} t_1 = 0.787 \text{ (rad)} \cong 45^\circ$. For $t=0$ we have $i(0)=5\text{A}$, which means $5 = i_m \sin 0.787$, and $i_m = 7.071 \cong 5\sqrt{2} \text{ (A)}$. Finally, the instantaneous current is: $i(t) = 7.071 \sin(314t + 45^\circ) = 5\sqrt{2} \sin(314t + 45^\circ) \text{ (A)}$.

Example 3.2.1. The sinusoidal current through a 5Ω 's resistance is: $i(t) = 2\sqrt{2} \sin(100t + 60^\circ)$ A. Calculate the rms value and instantaneous value of the voltage on the resistor. Find the value of the current and voltage for $t=0.01$ s.

Solution:

According to the relation between the current and voltage on a resistance, the rms value of the voltage is $U_R = I \cdot R = 2 \cdot 5 = 10$ (V), and the instantaneous voltage $u_R(t) = R \cdot i(t) = 10\sqrt{2} \sin(100t + 60^\circ)$ (V). The value of the current for $t=0.01$ s is $i(0.01) = 2\sqrt{2} \sin(1 + \frac{\pi}{3}) = 2.51$ (A), while the voltage value is $u(0.01) = 10\sqrt{2} \sin(1 + \frac{\pi}{3}) = 12.57$ (V).

Example 3.2.2. The sinusoidal current through a 250 mH's inductance is $i(t) = 4\sqrt{2} \sin(100t - 30^\circ)$ A. Calculate the rms value and the instantaneous value of the voltage on the inductance.

Solution:


The inductive reactance is $X_L = \omega L = 25 \Omega$. As a remark, the inductive reactance depends on the inductance but also on the angular frequency of the supplying current. The rms value of the voltage is $U_L = X_L \cdot I = 100$ (V), and the instantaneous voltage is $u_L(t) = L \frac{di}{dt} = 100 \sqrt{2} \cos(100t - 30^\circ) = 100 \sqrt{2} \sin(100t + 60^\circ)$ (V).

Example 3.2.3. The sinusoidal voltage across a $10 \mu\text{F}$'s capacitance is $u_C(t) = 150\sqrt{2} \sin(20t + 15^\circ)$ V. Calculate the rms value and the instantaneous value of the current through the capacitance.

Solution:

The capacitive reactance is $X_C = \frac{1}{\omega C} = 50 \Omega$. As a remark, the same as for the inductance, the capacitive reactance depends on the capacitance but also on the angular frequency of the supplying current. The rms value of the current is $I = \frac{U_C}{X_C} = 3$ (A), and the instantaneous voltage is $i(t) = C \frac{du_C}{dt} = 3\sqrt{2} \cos(20t + 15^\circ) = 3\sqrt{2} \sin(20t + 105^\circ)$ (A).

Example 3.3.1. The circuit parameters for the RC series circuit below are $R=100\Omega$, $C=31.8\ \mu\text{F}$. We know the current amplitude $i_m=1.41\text{ A}$ and the phase angle $\phi_i=0$. Determine: a) the instantaneous voltage on the capacitance, $u_c(t)$; b) the instantaneous voltage on the resistance, $u_R(t)$.

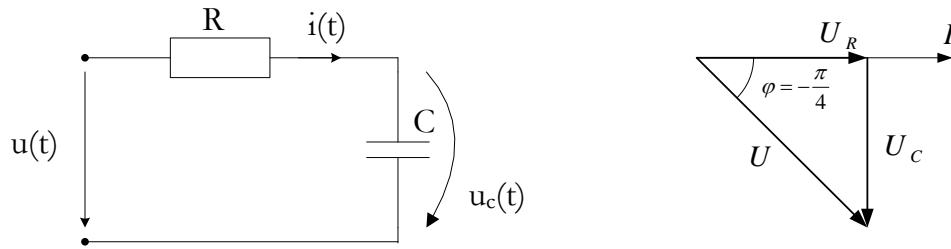


Example 3.3.1.

Solution:

The form of the sinusoidal current is: $i(t) = i_m \sin \omega t$. We can calculate the circuit impedance, $Z = \sqrt{R^2 + \left(-\frac{1}{\omega C}\right)^2} = 141.4\ (\Omega)$, and the supplying voltage amplitude, $u_m = Z \cdot i_m = 200\text{ (V)}$. From $\tan \varphi = \frac{-X_C}{R} = -\frac{1}{\omega RC} \cong -1$, the voltage phase angle is $\varphi = -45^\circ$. The instantaneous value of the supplying voltage is $u(t) = 200 \sin\left(100\pi t - \frac{\pi}{4}\right)\text{ (V)}$. The peak of the capacitance-voltage is $u_{Cm} = i_m \frac{1}{\omega C} = 141.13\text{ (V)}$ and the instantaneous voltage on capacitance is $u_c(t) = 141.13 \sin\left(100\pi t - \frac{\pi}{2}\right)\text{ (V)}$. The pick of the resistance voltage is $u_{Rm} = i_m R = 141\text{ (V)}$ and the instantaneous voltage on the resistance is $u_R(t) = 141 \sin(100\pi t)\text{ (V)}$. We take into account that the voltage on capacitance lags the current by an angle of 90° , while the voltage on the resistance is in phase with the current. The phasor diagram was drawn in the figure above.

Example 3.3.2. The circuit parameters for the RL series circuit below are $R=10\Omega$, $L=100$ mH, and the instantaneous voltage on the inductance $u_L(t) = 100 \sin(314t + 30^\circ)$ V. Determine: a) the instantaneous value of the current in the circuit, $i(t)$; b) the instantaneous value of the supplying voltage, $u(t)$.

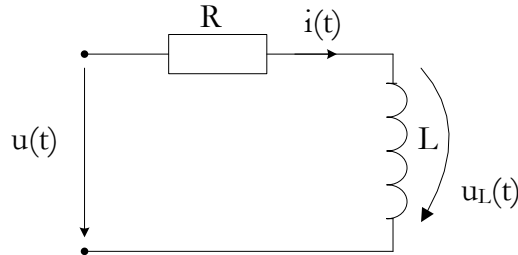


Example 3.3.2.

Solution:

At first, from $u_{Lm} = i_m \cdot X_L$ we calculate $i_m = \frac{u_{Lm}}{X_L} = 3.183$ A. The current lags the voltage on the inductor by an angle of 90° , $i(t) = 3.183 \sin(314t + 30^\circ - 90^\circ) = 3.183 \sin(314t - 60^\circ)$ (A). The circuit impedance is $Z = \sqrt{R^2 + (\omega L)^2} = 33$ (Ω), and the peak of the supplying voltage $u_m = Z \cdot i_m = 105$ (V). From $\tan \varphi = \frac{X_L}{R} \cong 3.14$, the phase angle between the supplying voltage and current is $\varphi = \arctan 3.14 \cong 72^\circ$. The voltage leads the current by the angle of 72° and, as a consequence, the instantaneous supplying voltage is $u(t) = 105 \sin(314t + 12^\circ)$ V.


Example 3.3.3. The circuit parameters for the RLC series circuit below are $R=40\Omega$, $L = \frac{6}{10\pi} H$, $C = \frac{1}{3\pi} \mu F$, and the supplying voltage: $u(t) = 100\sqrt{2} \sin(100\pi t - 60^\circ) V$. Calculate: a) inductive and capacitive reactance and the impedance of the circuit, X_L , X_C , Z ; b) rms and instantaneous value of the current, I , $i(t)$; c) rms and instantaneous value of the voltage on the resistance, U_R , $u_R(t)$; d) rms and instantaneous value of the voltage on inductance, U_L , $u_L(t)$; rms and instantaneous value of the voltage on the capacitance, U_C , $u_C(t)$.

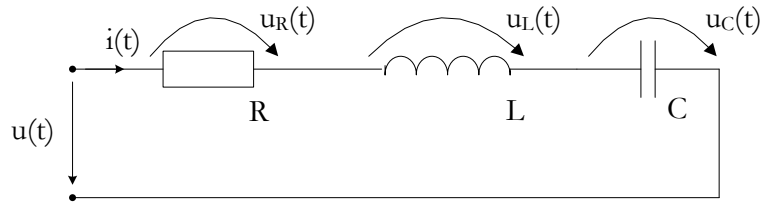

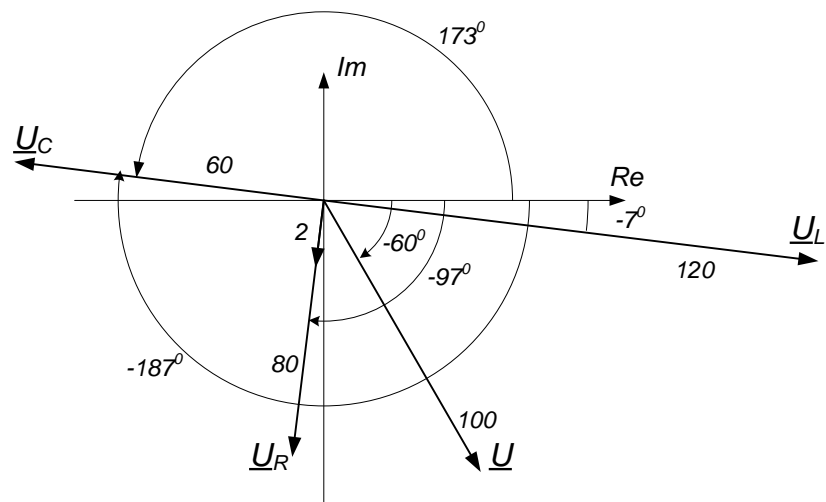
Example 3.3.3.

Solution:

The inductive reactance is $X_L = \omega L = 60 \Omega$, the capacitive reactance $X_C = \frac{1}{\omega C} = 30 \Omega$, and the circuit impedance $Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = \sqrt{R^2 + (X_L - X_C)^2} = 50 \Omega$. The rms value of the current is $I = \frac{U}{Z} = 2 A$, and from $\tan \varphi = \frac{X_L - X_C}{R} = \frac{3}{4}$, the phase angle between supplying voltage and current is $\varphi = \arctan \frac{3}{4} \cong 37^\circ$. Because $X_L > X_C$, the circuit behaves inductively, i.e. the current lags the voltage by the angle $\varphi = 37^\circ$. The instantaneous value of the current is $i(t) = 2\sqrt{2} \sin(100\pi t - 60^\circ - 37^\circ) = 2\sqrt{2} \sin(100\pi t - 97^\circ) (A)$. The rms value of the resistance voltage is $U_R = I \cdot R = 80 V$, and the instantaneous value $u_R(t) = 80\sqrt{2} \sin(100\pi t - 97^\circ) V$. The rms value of the inductance voltage is $U_L = X_L \cdot I = 120 V$, and the instantaneous value $u_L(t) = 120\sqrt{2} \sin(100\pi t - 7^\circ) V$ (the voltage on the inductance lags the current by an angle of 90°). The rms value of the capacitance-voltage is $U_C = X_C \cdot I = 60 V$, and the instantaneous value $u_C(t) = 60\sqrt{2} \sin(100\pi t - 187^\circ) V$ (the voltage on the capacitance leads the current by an angle of 90°).



Phasor Diagram

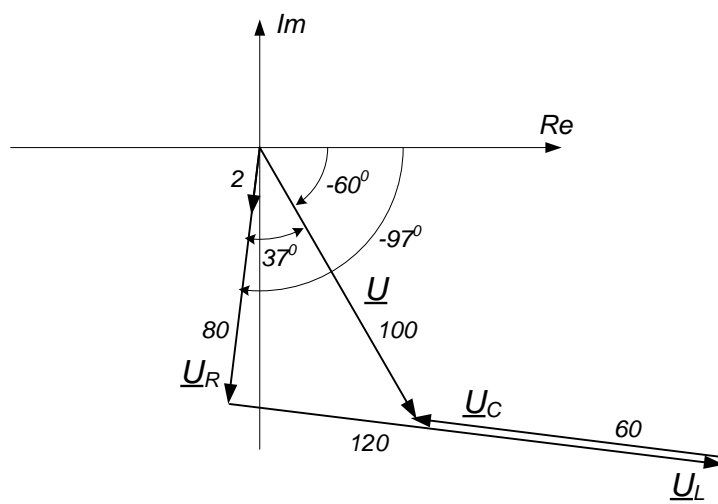

Phasor Diagram
